

This question paper contains 4 printed pages]

ND—22—2023

FACULTY OF SCIENCE AND TECHNOLOGY

B.Sc. CS (First Year) (First Semester) EXAMINATION

NOVEMBER/DECEMBER, 2023

(CBCS/Revised Pattern)

COMPUTER SCIENCE

Paper BCS-104 B

(Fundamentals of Digital Electronics)

(Wednesday, 6-12-2023)

Time : 10.00 a.m. to 1.00 p.m.

Time—3 Hours

Maximum Marks—75

N.B. :— (i) All questions are compulsory.

(ii) Figures to the right indicate full marks.

(iii) Assume suitable data, if required.

(iv) Use of any electronic media such as mobile phone, digital diary and electronic calculator is not permitted.

1. Attempt any *five* of the following (3 marks each) :

15

(a) Gray Code

(b) Half Adder

P.T.O.

WT

(2)

ND—22—2023

- (c) One's Complement of Binary
- (d) Hexadecimal number system.
- (e) Encoder
- (f) Ex-OR Gate
- (g) T flip-flop.

2. Attempt any *three* of the following (5 marks each) :

15

(a) Perform the following conversions :

(i) $(37)_{10} = (?)_2$

(ii) $(10101.01)_2 = (?)_{10}$

(iii) $(253)_8 = (?)_{16}$

(iv) $(D0E)_{16} = (?)_2$

(v) $(1632)_{10} = (?)_{16}$

(b) Perform the following Operations :

(i) $(1011)_2 + (11011)_2$

(ii) $(11000)_2 - (1011)_2$

(iii) $(111)_2 \times (101)_2$

(iv) $(1010)_2 \div (10)_2$

(v) $(10110)_2 = (?)_2$'s Complement

WT

(3)

ND—22—2023

- (c) What is Logic Gate ? Explain AND, OR and NOT Gates in detail.
- (d) What is Number System ? Explain Binary and Octal number systems in detail.
- (e) What is Parity Checking ? Explain Hamming code in detail.
3. Attempt any *three* of the following (5 marks each) : 15
- (a) Explain NAND and NOR Gates in detail.
- (b) State and prove DeMorgan's first and second theorem.
- (c) Minimize the following using K-map :
- $$f(A,B,C,D) = \sum m(0, 1, 2, 4, 5, 7, 8, 9, 10, 11, 14, 15)$$
- (d) Minimize the following using K-map :
- $$f(A,B,C,D) = \pi M (1, 2, 3, 5, 6, 8, 9, 12, 13, 14)$$
- (e) Draw the logic circuit for the following expression
- $$Y = A'B'C' + C' + (A.B)' + (B+C)'$$
4. Attempt any *three* of the following (5 marks each) : 15
- (a) Explain SOP and POS forms of the expression in detail.
- (b) What is Multiplexer ? Explain 8 : 1 Multiplexer in detail.
- (c) What is flip-flop ? Explain J-K flip-flop in detail.

P.T.O.

WT

(4)

ND—22—2023

- (d) What is Analog to digital converter ? Explain any *one* type of Analog to digital converter in detail.
- (e) What is Shift register ? Explain SISO and SIPO shift registers in detail.
5. Write short notes on any *three* of the following (5 marks each) : 15
- (a) BCD code
- (b) K-map
- (c) Full adder
- (d) D flip-flop
- (e) Asynchronous Counter.

ND—22—2023

4