

This question paper contains 2 printed pages]

**NY—160—2023**

**FACULTY OF SCIENCE**

**M.Sc. (First Year) (First Semester) EXAMINATION**

**NOVEMBER/DECEMBER, 2023**

**(New/CBCS Pattern)**

**PHYSICS**

**PHY-104**

**(Electronic Devices and Applications)**

**(Saturday, 9-12-2023)**

**Time : 10.00 a.m. to 1.00 p.m.**

*Time—3 Hours*

*Maximum Marks—75*

*N.B. :— (i) All questions are compulsory.*

*(ii) Figures to the right indicate full marks.*

1. What is SCR ? Explain construction and characteristics for it. 15

*Or*

(a) Give classification based on band gap of materials and discuss semiconductors in brief. 8

(b) What is BJT ? Explain working of NPN transistor in FR bias. 7

2. Explain in detail the construction, working principle and I-V characteristics of solar cell. 15

*Or*

(a) Explain construction and working of light emitting Diode. 8

(b) Explain the construction and working of photodiode. 7

P.T.O.

3. With a neat circuit diagram, explain op-amp as an integrator and differentiator.

15

*Or*

(a) Explain construction and working of op-amp as a non-inverting amplifier.

8

(b) State ideal characteristics of op-amp.

7

4. What is flip-flop ? Discuss symbol, working and truth table of J-K, T and D-type flip-flop.

15

*Or*

(a) What do you mean by multiplexer ? With logic diagram and truth table explain 4 : 1 multiplexer.

8

(b) With logic symbol and truth table explain basic logic gates.

7

5. Write short notes on any *three* :

15

(a) p-type semiconductor

(b) Direct and indirect band gap of semiconductor

(c) Op-amp as a comparator

(d) Shift register.